

Algebra Booleana Thais Ferreira Casquero

10403263

Estado atual	Estado futuro	Saídas atuais dos flip flops			Saídas futuras flip flops			Entradas		
		Qc	Qb	Qa	Qc	Qb	Qa	Dc	Db	Da
0	1	0	0	0	0	0	1	0	1	
1	3	0	0	0	0	1	1	0	1	
2	6	0	0	1	0	1	0	1	0	
3	2	0	1	0	1	1	0	0	0	
4	0	0	1	1	0	1	0	0	0	
5	4	1	0	0	0	0	0	0	0	
6	7	1	0	1	1	0	0	1	0	
7	5	1	1	0	1	1	1	1	1	
		1	1	1	1	0	1	1	1	

QB QA					Qc QB QA				
DB	00	01	11	10	DA	00	01	11	10
Qc	0	0	1	1	1	0	1	1	0
Qb	1	0	0	0	1	0	0	0	1
Qa	1	0	0	1	1	0	0	1	1

$$Dc = Qc \cdot Qa + Qb \cdot \bar{Qa}$$

$$Db = \bar{Qc} \cdot Qa + Qb \cdot \bar{Qa}$$

$$Da = \bar{Qc} \cdot \bar{Qb} + Qc \cdot Qb$$

